


COSC175 (Systems I): Computer Organization & Design

Professor Lillian Pentecost
Fall 2024



Warm-Up September 12

- Where we were
 - Picking up with simplifying boolean equations and proving equality
 - Describing simple circuits in SystemVerilog
- Where we are going
 - Even more tools for simplification, more examples, a fan favorite: **K-Maps**
- Logistics, Reminders
 - Evening help sessions 7-9PM on Sundays, Tuesdays, Thursdays in C107
 - LP Office Hours at 2:30-4PM Today, CANCELED on Monday
 - Weekly Exercises Due Friday 5PM
 - Lab 1 due Monday 10PM
 - **Thank you to our volunteers, the lab sections are more balanced now!**
- Textbook Tags: 2.4, 2.5, 2.6, 2.7

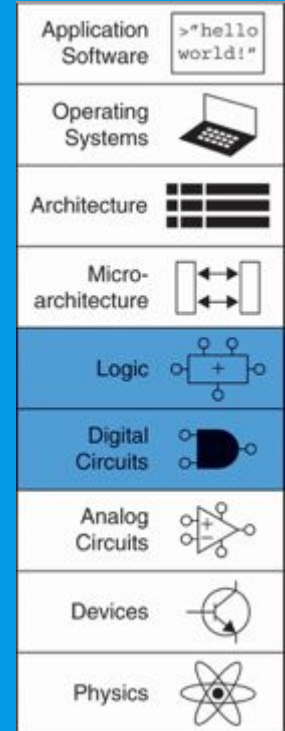

Day2 Check-In (Recap)

- A. Prove T9 (**covering**) theorem using each method (TT, other theorems)
- B. Simplify the following expressions into **two or fewer terms**, each with **two or fewer literals**, then check your work with a truth table:
- a. $Y = AC + BC + ABC$
- b. $Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + \overline{(A + \bar{C})}$

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{\overline{B}} = 0$	$B + \overline{\overline{B}} = 1$	Complements

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B+C = C+B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B+C) (B+D)$	<u>Distributivity</u>
T9	$B \bullet (B+C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B+C) \bullet (B+\bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B+C) \bullet (\bar{B}+D) \bullet (C+D) = (B+C) \bullet (\bar{B}+D)$	Consensus
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B+C+D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's

Simplify B.b together on board

Define Minimization: **depends on your priorities!** For a boolean equation, we would aim for a sum of fewest, simplest possible implicants (or products), but for a circuit, we might want to minimize **total number of gates**, or **eliminate certain types of gates**, or **reduce the “depth”** of the circuit, to make it optimal.

b. $Y = \bar{A}\bar{B} + \bar{A}B\bar{C} + \overline{(A + \bar{C})}$

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{\overline{B}} = 0$	$B + \overline{\overline{B}} = 1$	Complements


#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B+C = C+B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B+C) (B+D)$	<u>Distributivity</u>
T9	$B \bullet (B+C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B+C) \bullet (B+\bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B+C) \bullet (\bar{B}+D) \bullet (C+D) = (B+C) \bullet (\bar{B}+D)$	Consensus
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B+C+D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's

Organized Gate Schematics using PLAs

Programmable Logic Arrays are a general structure for constructing canon form schematics, making translating SOP, for example, very straightforward!

See DDCA 2.4, 2.5 for more tips and structures for schematics!

 Example: $Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}C$



D, X, and Z as Values?

D for a “**Don’t Care**” value in the development of a design


X for an **illegal value**, the result of a contentious or unclear operation

Z for a **floating value**, not knowably 0 or 1 or somewhere in between

“Don’t Care”s in Truth Tables: Example

Imagine a **priority circuit**: Output of
“1” corresponding to most significant
“1” input


... starting with the truth table

 

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				


“Don’t Care”s in Truth Tables: Example

 Imagine a **priority circuit**: Output of
“1” corresponding to most significant
“1” input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

“Don’t Care”s in Truth Tables: Example

 

Imagine a **priority circuit**: Output of “1” corresponding to most significant “1” input

... we will use a “D” or an “X” in a truth table to denote “don’t care”

Remember your majority vote circuit
– are there any potential “Don’t Care”s in that behavior?

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	x	0	0	1	0
0	1	x	x	0	1	0	0
1	x	x	x	1	0	0	0

$$Y_3 = A_3$$


$$Y_2 = \overline{A_3} A_2$$

$$Y_1 = \overline{A_3} \overline{A_2} A_1$$

$$Y_0 = \overline{A_3} \overline{A_2} \overline{A_1} A_0$$

Contention: X


- **Contention:** circuit tries to drive output to 1 and 0
 - Actual value somewhere in between
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation
- **X is also used for:**
 - Uninitialized values
 - Don't Care
- **Warnings:**
 - Contention or uninitialized outputs usually indicate a **bug**.
 - Look at the context to tell meaning

 

Floating: Z

- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter **won't** indicate whether a node is floating
 - But if you touch the node or wait a while, it may change values


Tristate Buffer

 

<i>E</i>	<i>A</i>	<i>Y</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

Tristate Busses for mediating components

 - Floating nodes are used in tristate busses
 - Many different drivers
 - Exactly one is active at once



Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations **graphically** and **efficiently**
- Multi-bit inputs are listed in **gray code** ordering

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
Y	C	0	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
Y	C	0	0	0	0
	1	1	0	0	0

Making K-Maps Useful

- Circle 1's in adjacent squares
- In groups of 1, 2, 4, 8... (powers of two)

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

		AB			
		00	01	11	10
Y	C				
		0	1	1	0
	0	1	0	0	0
	1	1	0	0	0

		AB			
		00	01	11	10
Y	C				
		0	1	1	0
	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

3-Input K-Map

- Circle 1's in adjacent squares
- In Boolean expression: include only literals whose true **and** complement form are **not** in the circle

Truth Table			
A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

		K-Map			
Y C	AB	00	01	11	10
0		0	1	0	0
1		0	1	1	0

$$Y = \bar{A}B + BC$$

Rules for K-Map Minimization

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**


Crank it up!! 4-input example

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Y CD \ AB					
		00	01	11	10
0	00	1	0	0	1
	01	0	1	0	1
	11	1	1	0	0
	10	1	1	0	1

Crank it up!! 4-input example

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

 

$$Y = \bar{A}\bar{C} + \bar{A}\bar{B}\bar{D} + \bar{A}BD + \bar{B}\bar{D}$$

... Now let's add another rule

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**
- Circle a ***“don't care” (D)*** ***only if it helps*** minimize the equation


“Don’t Care”s in K-Maps

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

<i>Y</i> <i>CD</i>	<i>AB</i>			
	00	01	11	10
00	1	0	X	1
01	0	X	X	1
11	1	1	X	X
10	1	1	X	X

“Don’t Care”s in K-Maps

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

 

$$Y = A + \bar{B}\bar{D} + C$$

Wrap-Up September 12



- Coming up next!
 - Bigger, better, multi-component designs → **building computational units**
 - ***On your own: be sure to read DDCA 2.4 and 2.5 to inform your designs and schematic drawing!***
- Logistics, Reminders
 - Evening help sessions 7-9PM on Sundays, Tuesdays, Thursdays in C107
 - LP Office Hours at 2:30-4PM Today, CANCELED on Monday
 - Weekly Exercises Due Friday 5PM
 - Lab 1 due Monday 10PM (**you have keycard access to C107, the laptops and FPGAs must stay in that room at all times, no propping door open, clean up when you leave**)
 - **Thank you to our volunteers, the lab sections are more balanced now!**
- FEEDBACK
 - <https://forms.gle/5Aafcm3iJthX78jx6>